
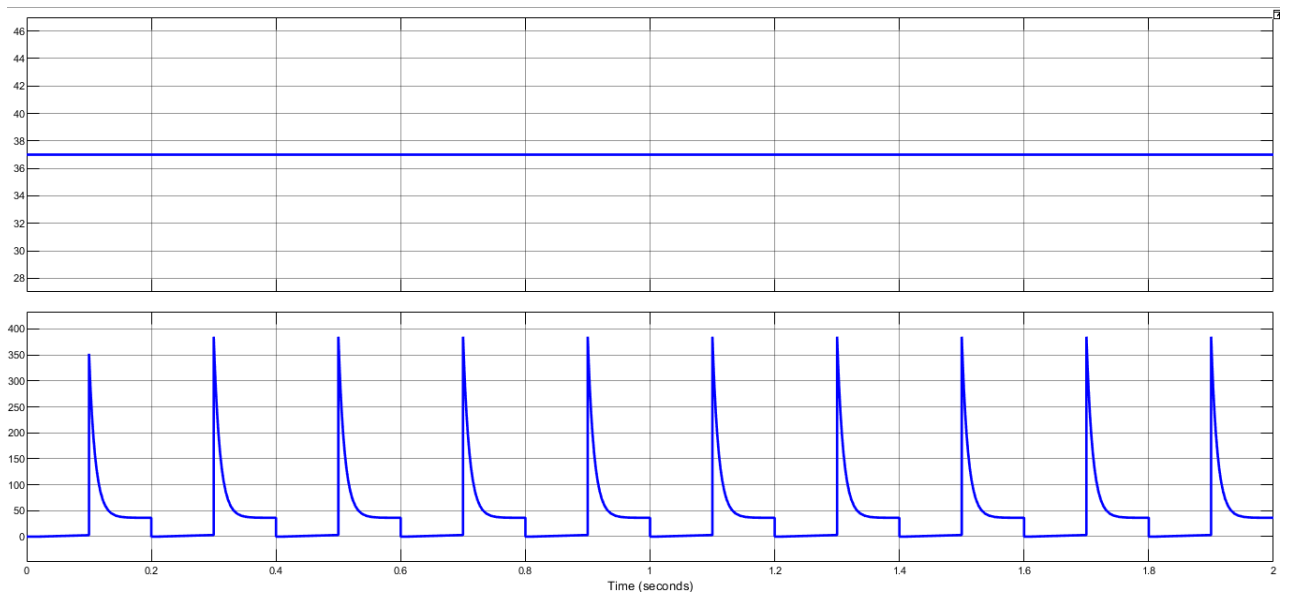


Continuous  
powergui
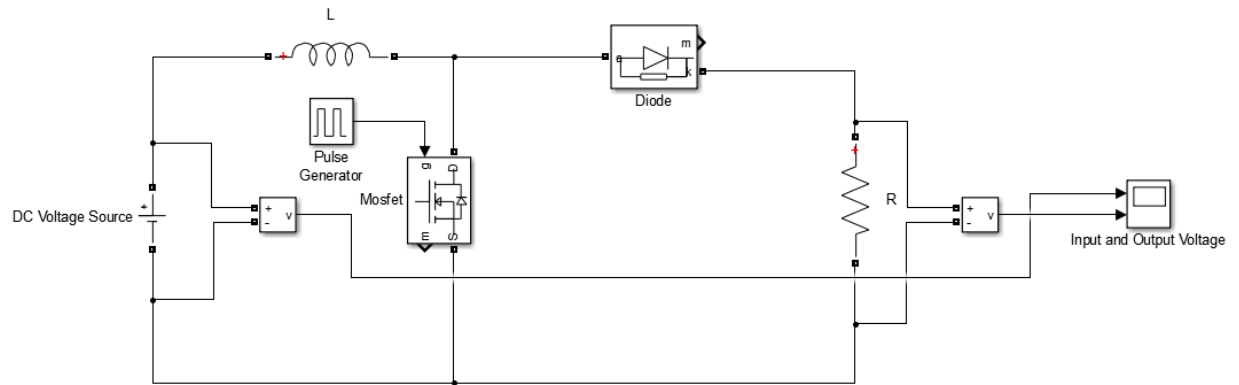
### 9(a). Simulation of DC-DC Boost Converter



### 9(b). Simulation of DC-DC Buck Converter

